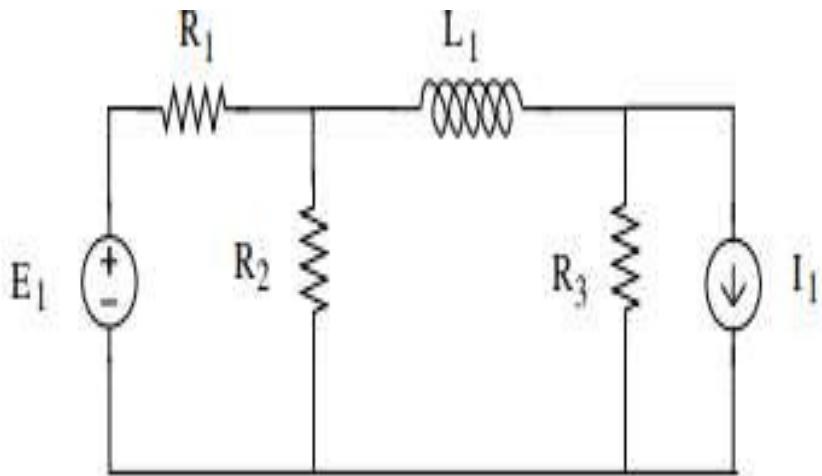


## **R-L and R-C DC Transient**

**CIRCUIT DIAGRAM and CALCULATIONS:**

**Problem 1:** Calculate the time constant for the given circuit.  $R_1=4$ ,  $R_2=8$ ,  $R_3=2$ ,  $L_1=3H$ ,  $E_1=3V$ ,  $I_1=2A$




**Solution:** Theoretical solution:


Handwritten notes on a notebook page:

- Given values:  $R_1 = 4\Omega$ ,  $L = 3H$ ,  $E_1 = 3V$ ,  $R_2 = 8\Omega$ ,  $R_3 = 2\Omega$ ,  $I_1 = 2A$
- Calculation of Thevenin resistance:  $\Sigma = \frac{L}{R_{TH}}$
- Equivalent circuit diagram showing the Thevenin source and load.
- Calculation of equivalent resistance:  $\frac{8}{13} \Omega$  and  $14/3 \Omega$ .
- Final calculation for time constant:  $\therefore \tau = \frac{L}{R} = \frac{3}{14} \times 3 \Rightarrow \frac{9}{14} = \underline{\underline{0.6428\text{sec}}}$


## Simulation: Circuit:

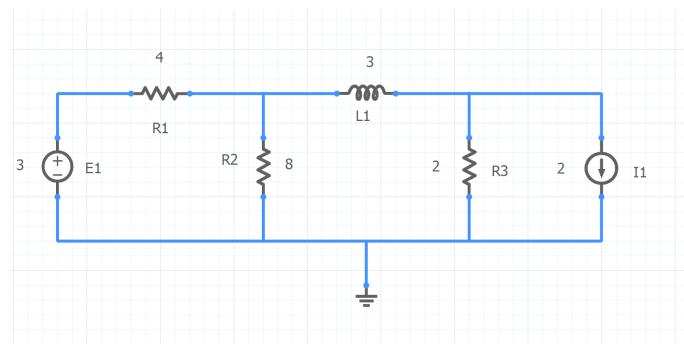

## Graph:

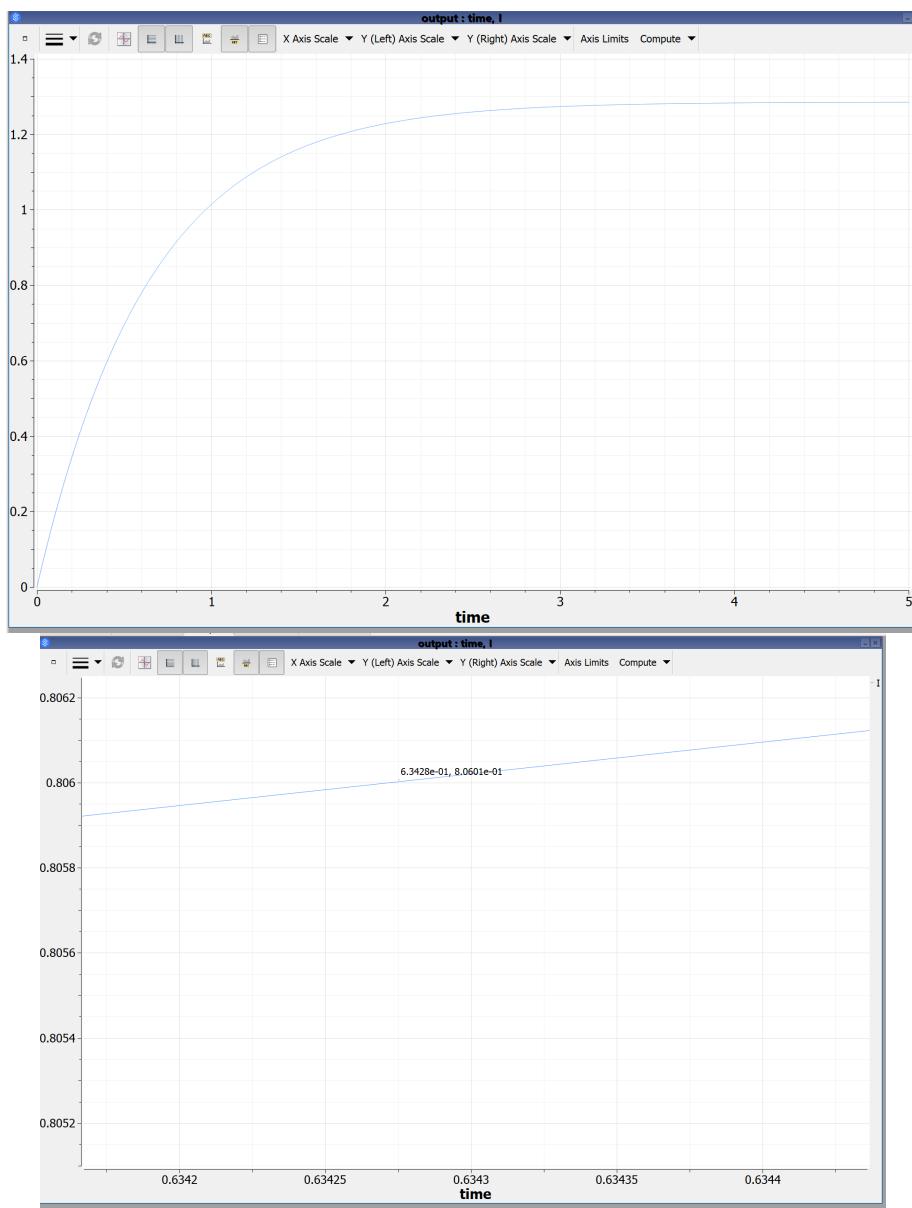

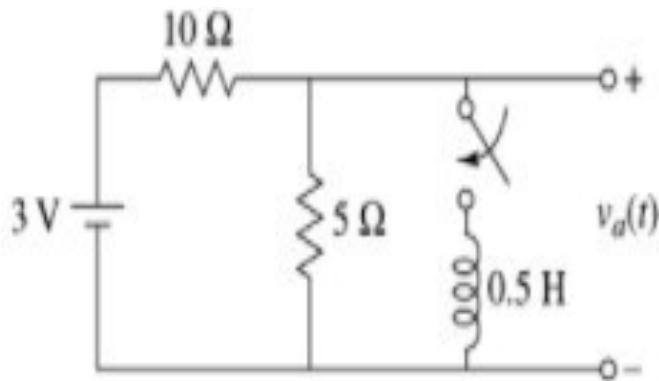**Problem 2.** Steady state is achieved with switch is open. At  $t=0$ , Switch is closed. Find  $v_a(t)$




**Solution:** Theoretical solution:



Handwritten notes and calculations for the circuit analysis:

- Initial state ( $t = 0^-$ ): The circuit has a steady state with a current  $i_f(0^-) = 0.3 \text{ A}$  flowing through the 10Ω resistor. The voltage across the inductor is  $V_f(0^-) = 0 \text{ V}$ .
- At  $t = 0^+$ , the switch closes, connecting the 5Ω resistor in series with the inductor. The initial current through the inductor is zero ( $i_{initial} = 0$ ).
- The total current  $i_a(t)$  is given by the equation:
$$i_a(t) = i_f(0^-) (1 - e^{-t/\tau}) + i_{initial} (e^{-t/\tau})$$
where  $\tau = \frac{L}{R_{TH}} = \frac{0.5}{\frac{10+5}{3}} = 0.15 \text{ s}$
- At  $t = \infty$ , the current  $i_f(\infty) = 0.3 \text{ A}$  and the voltage  $V_a(\infty) = 0 \text{ V}$ .
- The final voltage across the inductor is:
$$V_a(\infty) = L \frac{di}{dt} \Big|_{t=\infty} = 0.5 \times 0.3 \times e^{-\frac{t}{0.15}} \Big|_{t=\infty} = 0 \text{ V}$$


## Simulation: Circuit:

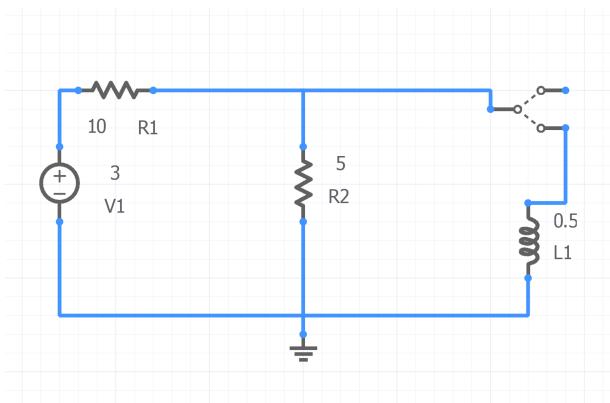

## Graph:

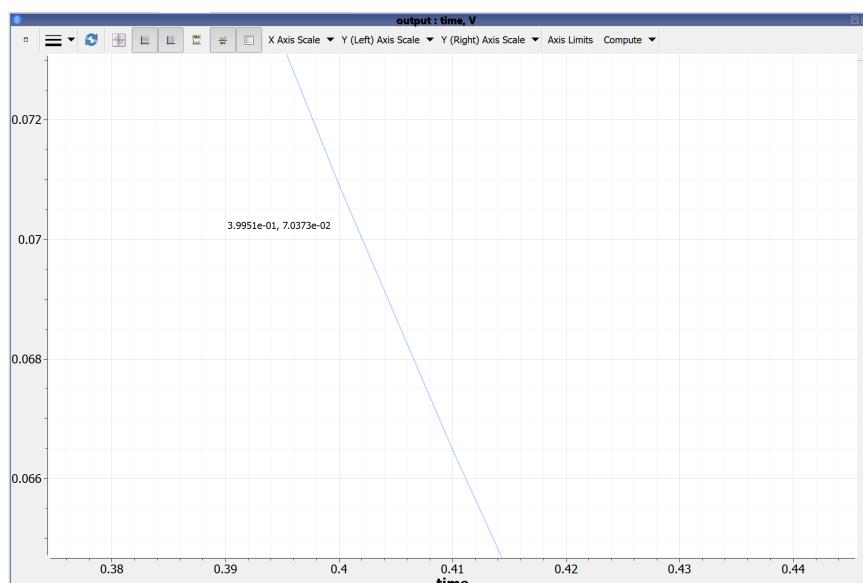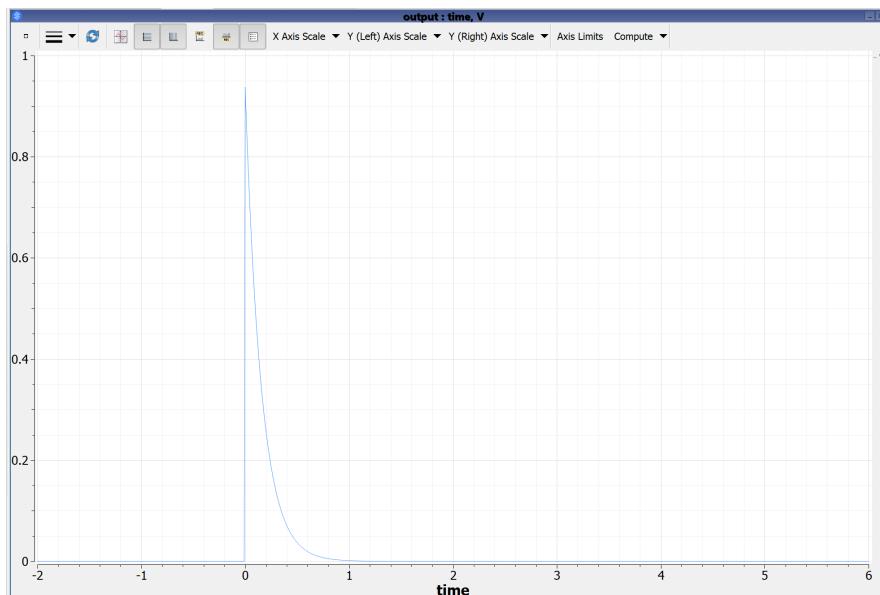

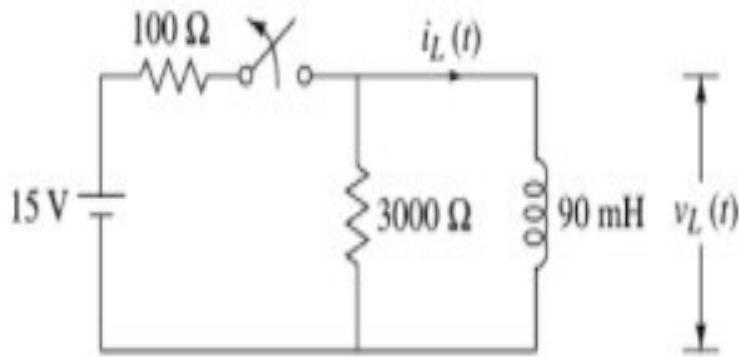**Problem 3:** Steady-state is reached with the switch closed. It is opened at  $t=0$ . Obtain  $i_L(t)$  and  $v_L(t)$



**Solution:** Theoretical solution:

Aug-20  
29 Monday

Q. 2]  $15V$   $100\Omega$   $i_L(t)$   $3000\Omega$   $90mH$   $v_L(t)$

solt:

$$R_{TH} = \frac{1}{100} + \frac{1}{3000}$$

$$R_{TH} = \frac{3000}{31} \approx R_{TH} = 96.77\Omega$$

$$T = \frac{L}{R} = \frac{90 \times 10^{-3}}{96.77} \times 31$$

$$= 9 \times 10^{-5} \times 31$$

$$= 9.3 \times 10^{-4} \text{ sec}$$

30 Tuesday

Now, ab t = 0

$15V$   $100\Omega$   $3000\Omega$   $90mH$

0.15A

Wednesday

0.15A  $96.77\Omega$   $90mH$

$14.516V$   $96.774\Omega$   $90mH$

$$i_{initial} = \frac{14.51}{96.77} = 0.15A$$


$i_{final} = 0$

Thursday


$$i(t) = 0.15e^{-\frac{t}{4.3 \times 10^{-4}}}$$

$$\therefore v(t) = 14.516 e^{-1075.068 t}$$


## Simulation: Circuit:

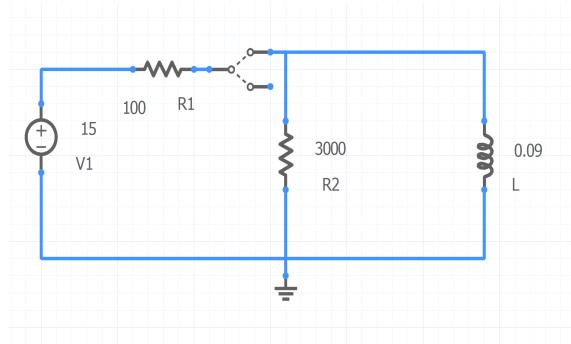

## Graph:

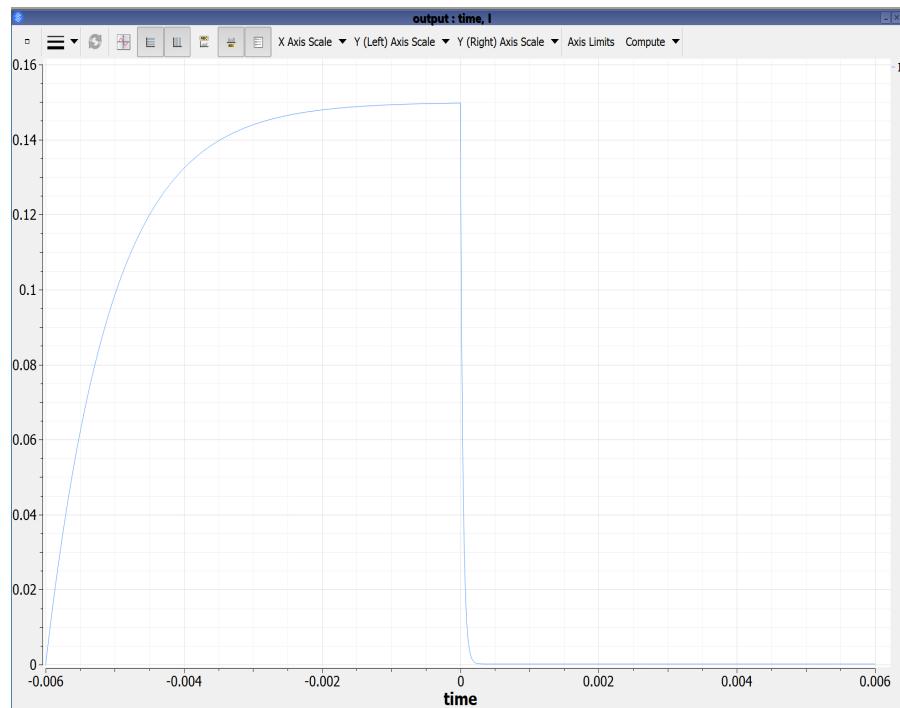

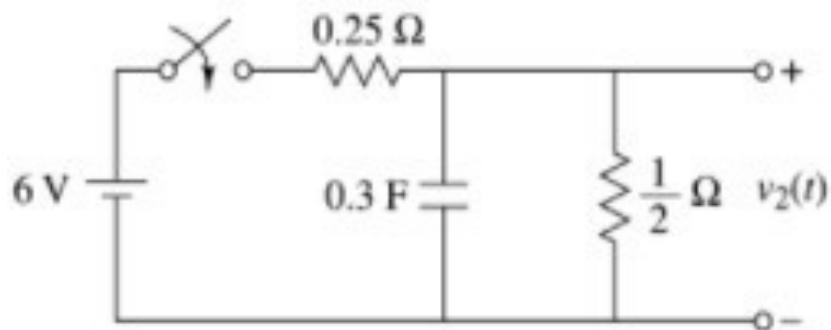**Problem 4:** The switch is open for a long time and closed at  $t=0$ . Determine  $v_2(t)$



**Solution:** Theoretical solution:

24 Wednesday

Q. 4]  $\frac{6V}{0.25\Omega}$   $\frac{0.3F}{\frac{1}{2}\Omega}$   $v_2(t)$

~~at  $t = 0^-$~~   $V_0 = 0$

$T = 0.3 \times R_{TH}$

$\frac{1}{0.25} + \frac{1}{0.3} = 4.33$

25 Thursday

$\frac{1}{0.25} = 4$

$\frac{1}{0.25} + \frac{1}{0.3} = 4.33$

$\therefore T = 0.3 \times \frac{1}{0.25} = \underline{\underline{0.05 \text{ sec}}}$

$V = Ae^{-\frac{t}{T}} + V_\infty$

$V = Ae^{-\frac{t}{0.05}} + 6$

at  $t = 0^-$   $V = 0$

$\therefore 0 = A + 6$


$\therefore A = -6$

[www.elleys.net](http://www.elleys.net)


$\therefore V_2(t) = 6(1 - e^{-20t})$


## Simulation:

### Circuit:

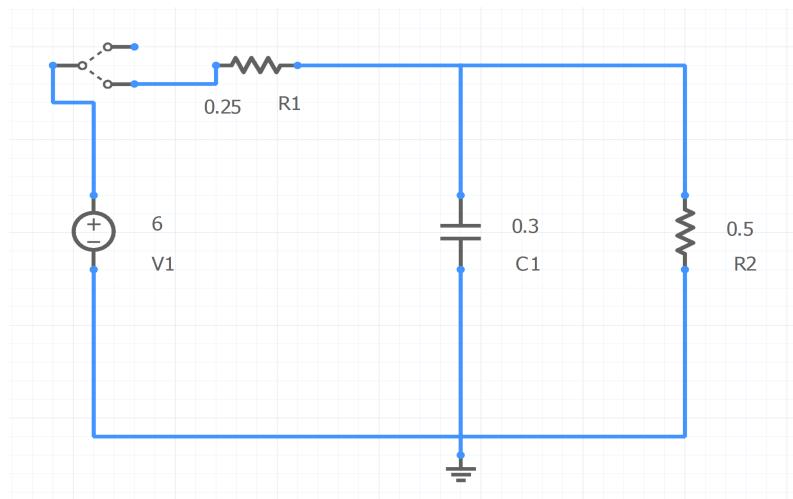


### Graph:

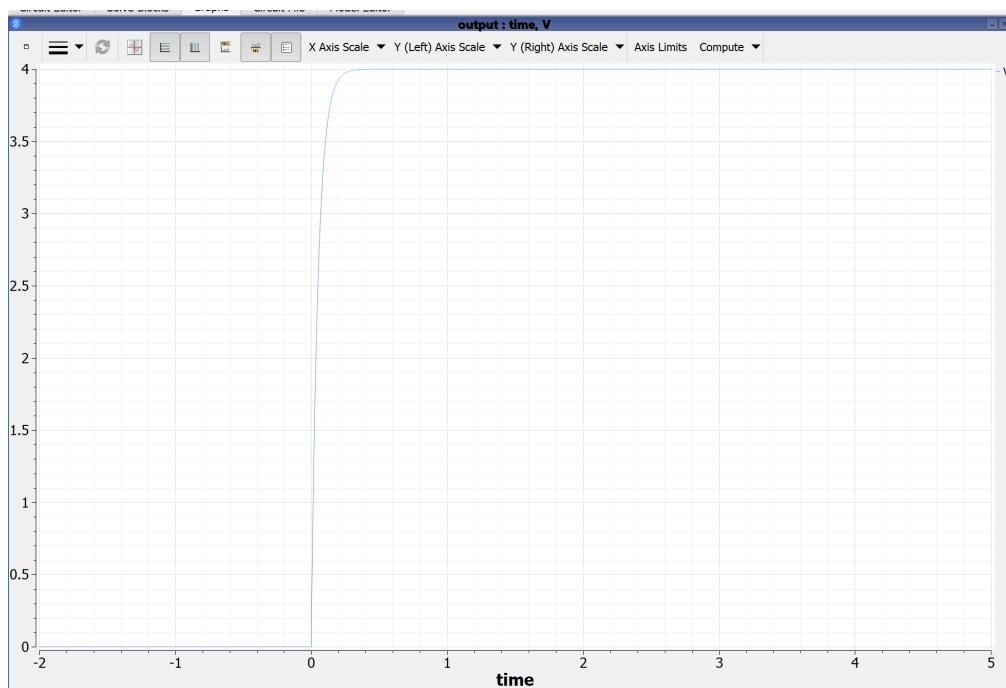

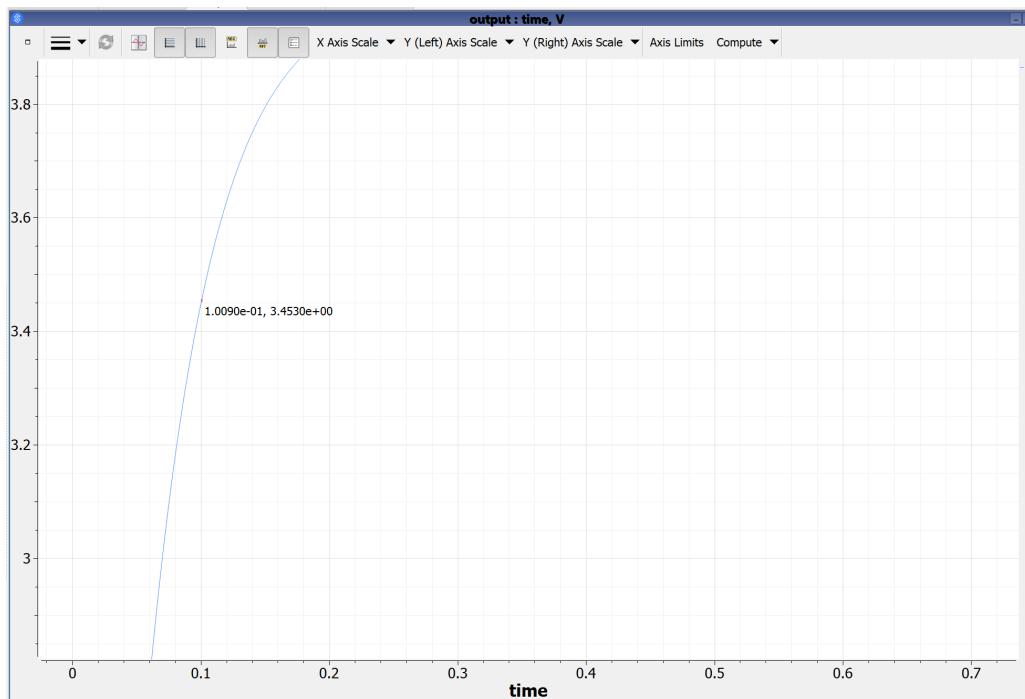

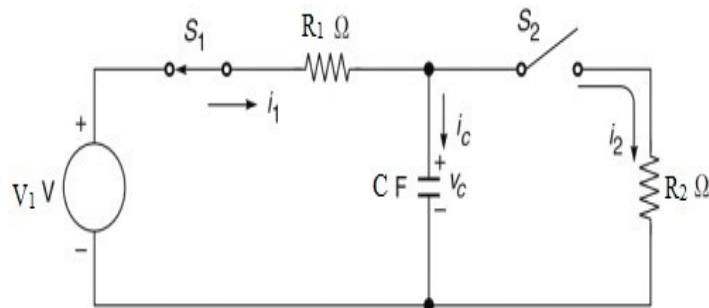**Problem 5:** Switch S<sub>1</sub> is closed for long time. At t=0 switch, S<sub>2</sub> is closed. Compute  $V_C$ .  $R_1=4$ ,  $R_2=4$ ,  $V_i=10$ ,  $C=1$



**Solution:** Theoretical solution:


Q.5]  $V_i = 10 \text{ V}$ ,  $C = 1 \text{ F}$ ,  $R_1 = 4 \Omega$ ,  $R_2 = 4 \Omega$   
 find  $V_C = ?$

Soln:-


$V_C(\text{ini}) = V_i = 10 \text{ V}$   
 at  $t = \infty$   
 $R_{TH} = 2 \Omega$   
 $T = 2$   
 $\therefore V_C(t) = 5(1 - e^{-\frac{t}{2}}) + 10e^{-\frac{t}{2}}$   
 $V_C(t) = 5(1 + e^{-\frac{t}{2}})$


## Simulation:

### Circuit:

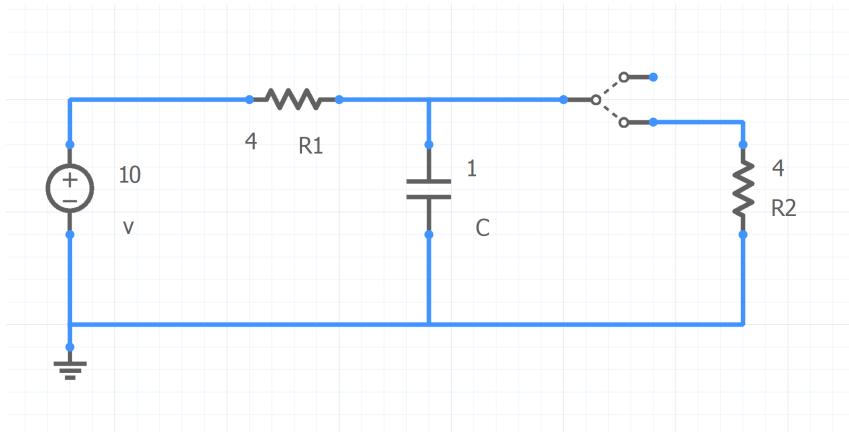

### Graph:

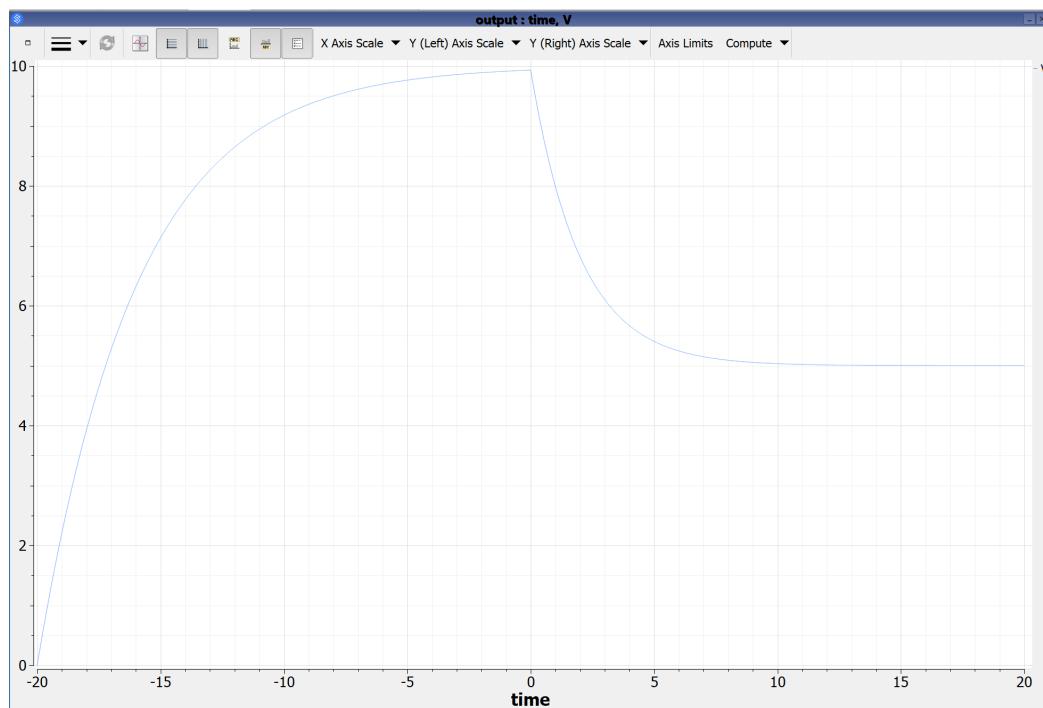

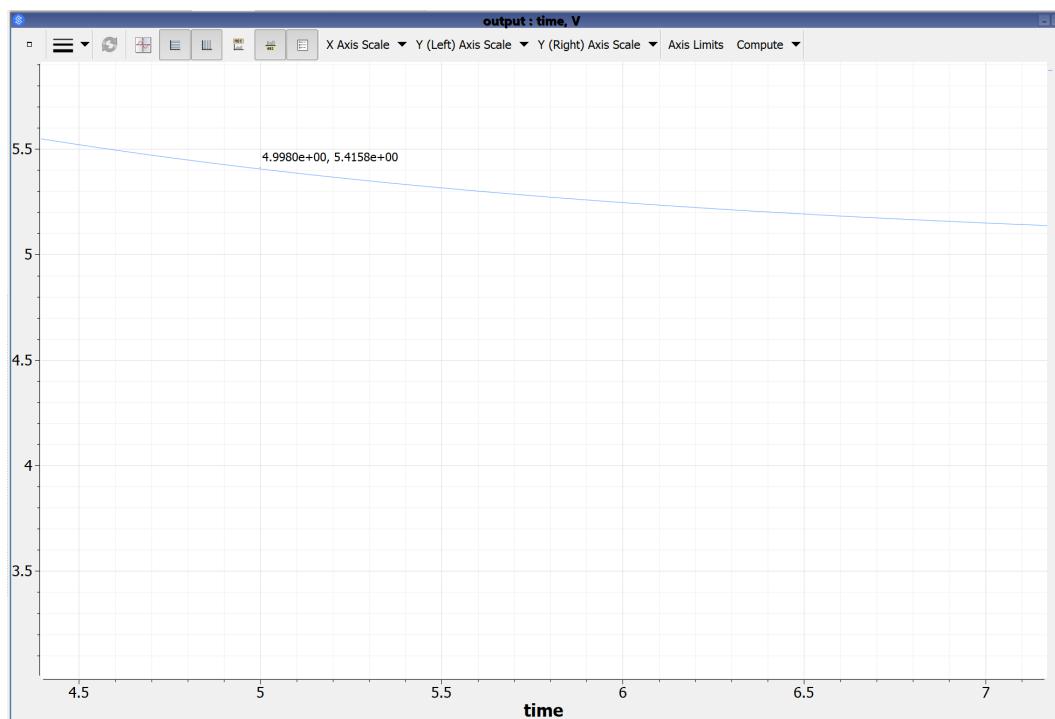

NAME: Pranay Singhvi EXPERIMENT No: 4

DATE: 28/06/ 2022

## R-L and R-C DC Transient response

**AIM:** To verify DC Transient response for the given R-L an R-C circuits.

**APPARATUS AND COMPONENTS REQUIRED:** Sequel Simulator

**THEORY: Write theory related with following questions:**

- 1) Define time constant, initial condition, final condition, transient response, natural response, forced response.

Ans:

1. Time constant: a time which represents the speed with which a particular system can respond to change, typically equal to the time taken for a specified parameter to vary by a factor of  $1 - 1/e$  (approximately 0.6321).
2. Initial Condition: Initial conditions in the circuit are the boundary values of the differential equation governing the circuit.
3. Final Condition: Final conditions in the circuit are the boundary values of the differential equation governing the circuit.
4. Transient response: A transient response of a circuit is a temporary change in the way that it behaves due to an external excitation, that will disappear with time. Damping oscillation is a typical transient response where the output value oscillates until finally reaching a steady-state value.
5. Natural response: The natural response of a circuit is what it does "naturally" as its internal energy moves around.
6. Forced response: Forced response is the system's response to an external stimulus with zero initial conditions.

### **PROCEDURE:**

- 1) Solve the problems given in below table (as per your batch e.g. X1= A1/B1/C1) to obtain transient response of R-L and R-C circuits
- 2) Verify the solution of the problems solved in step 1 using Sequel software.

### **RESULT:**

Problem no.	Parameter	Theoretical	Practical
1	Time Constant	0.6428 s	0.6348 s
2	V(t)	At t = 0.4s, V = 0.0694V	At t = 0.4 s, V = 0.0702 V

<b>3</b>	I(t)	At t = 0s, I = 0.15 A	At t = 0 s, I = 0.148 A
<b>4</b>	V(t)	At t = 1s, V = 3.2749V	At t = 1s, V = 3.5V
<b>5</b>	V(t)	At t = 5s, V = 5.41V	At t = 5s, V = 5.418 V

**CONCLUSION:**

We learned to find the time constant and we verified using simulink simulation. We also verified our current & voltage equation using simulink.